

Transistors, Gate Design and Properties


Brent C. Munsell

Computer Organization

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

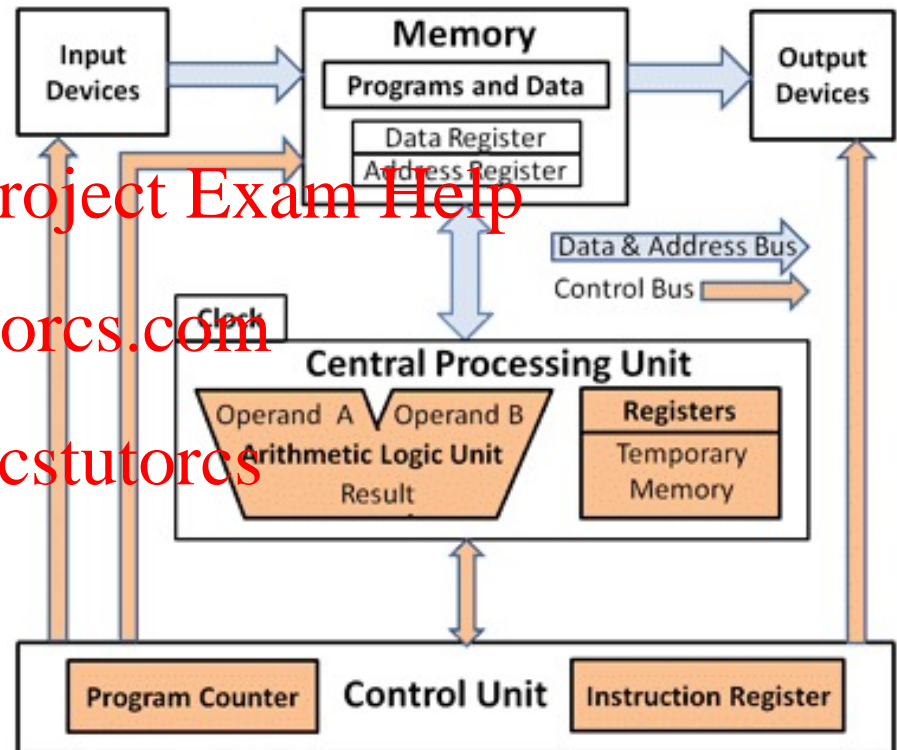

Agenda

- Announcements (~ 5 mins)
 - Poll Everywhere (~15 mins)
 - Complete ALU Material (~15 mins)
 - Transistors
 - Voltage and Logic
 - Propagation Delay
- Assignment Project Exam Help
<https://tutorcs.com>
WeChat: cstutorcs
- (~35 mins)

Announcements

- Lab 1
 - Due 9/15 @ 11:55 pm with no late penalty.
- Quiz 1
 - Great job (mean ~86%, mode 100%)!
 - Release grades and feedback today or tomorrow (talk to Jesse)
- Quiz 2
 - Release this Friday @ 12 pm
 - Due this Sunday @ 11:55 pm
 - Post announcement this Thursday.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Transistor

Overview, Design, and Operation

Overview


Schematic Diagram

 

Abstraction for humans



Transistor

 

Physical Hardware: Along with power (V_{CC}) and ground (GND), four transistors are required to make one two-input NAND gate

Transistor Size?

[Intel Video](#): Really good 😊



Three billion transistors on a fingertip. Credit: [Fritzchens Fritz](#)

Voltage (V_{CC}) and Ground (GND)

Think of a direct current (DC) battery:



Assignment Project Exam Help

(+) voltage DC

- e.g., $V_{CC} = 1.5 \text{ VDC}$ or 9 VDC (many other values)

<https://tutorcs.com>
WeChat: cstutorcs

(-) voltage DC

- E.g., GND or 0 VDC




Basic Design

Conceptually, a DC voltage switch!

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: estutorcs

 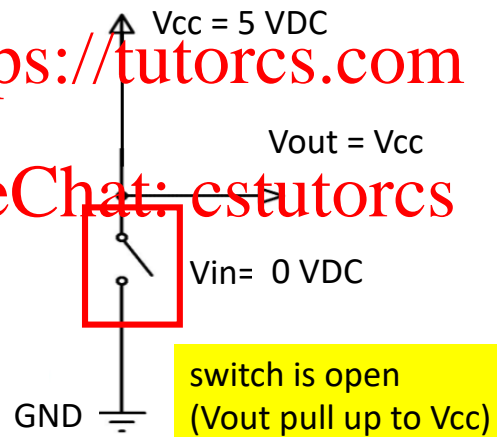 




Basic Operation

Let's work through a simple example

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

   

Input (V_{in}) voltage is "switching" the output (V_{out}) voltage

Metal Oxide Semiconductor (MOS) Transistor

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Complementary Pull-up/down Design

n-channel Metal Oxide Semiconductor (nMOS) Transistor


Switch is closed when gate (g) is positive VDC value (e.g., 5 VDC)

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: estutorcs

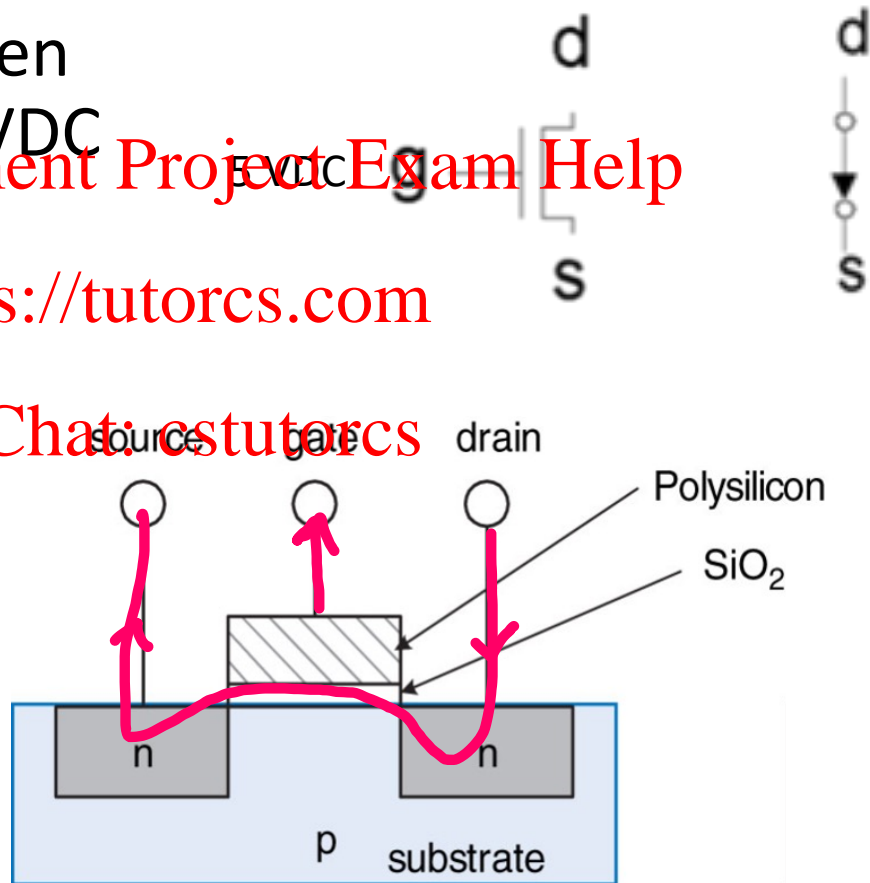Channel is open, electrons can flow from drain to source



n-channel Metal Oxide Semiconductor (nMOS) Transistor


Switch is open when gate (g) is GND (e.g., 0 VDC)

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

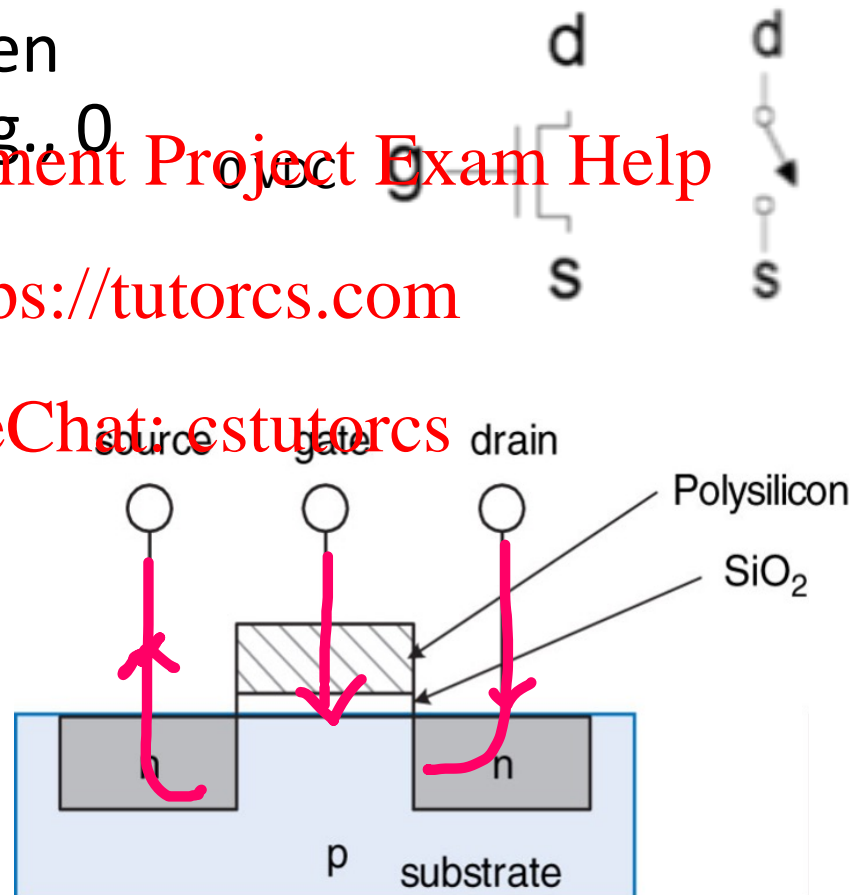Channel is closed, electrons cannot flow from drain to source




p-channel Metal Oxide Semiconductor (pMOS) Transistor

Switch is open when gate is positive VDC value (e.g., 5 VDC)

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: estutorcs

 

Channel is closed, electrons cannot flow from source to drain


p-channel Metal Oxide Semiconductor (pMOS) Transistor

Switch is closed when gate is GND (e.g., 0 VDC).


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 


 Channel is open, electrons can flow from source to drain.



NOT Gate MOS Gate Design

Schematic Diagram

 

Truth Table

$V_{cc} = 5 \text{ VDC}$

A	P1	N1	Y
GND	5 VDC	GND	5 VDC
5 VDC	GND	5 VDC	GND




Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Pull UP


Pull DOWN

   

Complementary MOS Design

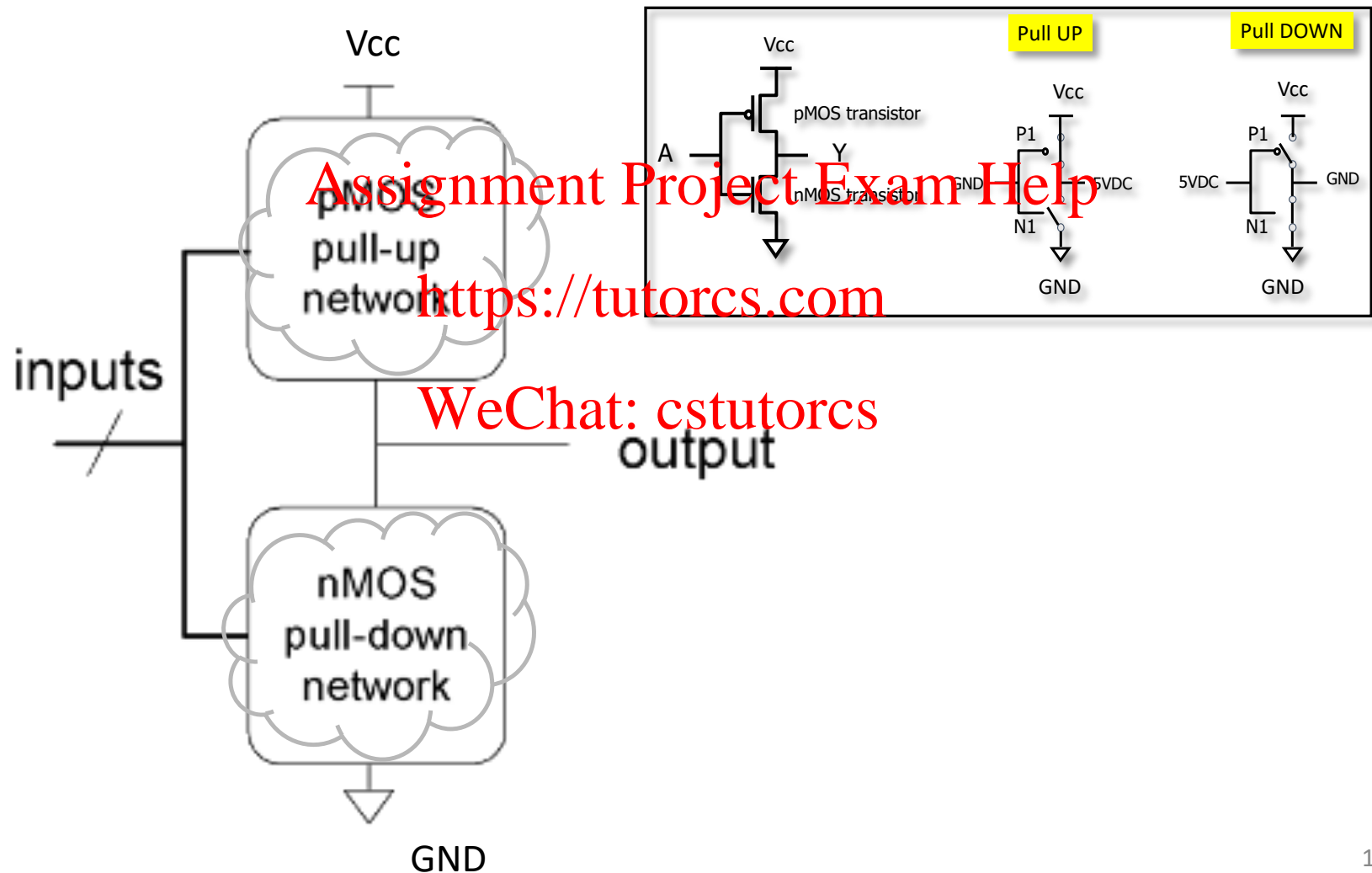

NAND Gate: MOS Design

 


A	B	P1	P2	N1	N2	Y
GND	GND	5VDC	5VDC	GND	GND	
GND	5VDC	5VDC	GND	GND	5VDC	
5VDC	GND	GND	5VDC	5VDC	GND	
5VDC	5VDC	GND	GND	5VDC	5VDC	


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 

NOR Gate: MOS Design

 

A	B	Y
GND	GND	
GND	5VDC	
5VDC	GND	
5VDC	5VDC	

Vcc = 5 VDC

Relationship between Voltage and Logic

Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Digital abstraction

Voltage and Logic

Voltage a continuous value

 - Has a defined range of values, e.g., 0 to 5 VDC
- And any VDC value between, e.g., 0.1, 0.11, 1.25, 4.52, etc.
- Hardware understands voltage values



Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Boolean Logic (or Logic for short) is a discrete value that can only be 0 or 1.

- Abstraction that humans understand
- Apply the rules of Boolean algebra
- Simplifies circuit design



Continuous to Discrete Conversion

Logic 1


- Voltage range 5 to 2 VDC

Logic 0

- Voltage range 0 to 0.8 VDC

Invalid

 - Less than 2 VDC and greater than 0.8 VDC
- Unstable and not reliable.



Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Why is a range of values acceptable?
Give an example, not related to voltage?

Assignment Project Exam Help

Component
Properties


<https://tutorcs.com>

WeChat: cstutorcs

Propagation delay


NOT Gate: Closer Inspection

 Output (Y) transitions from logic 0-to-1 (or 1-to-0)




Ideal Property

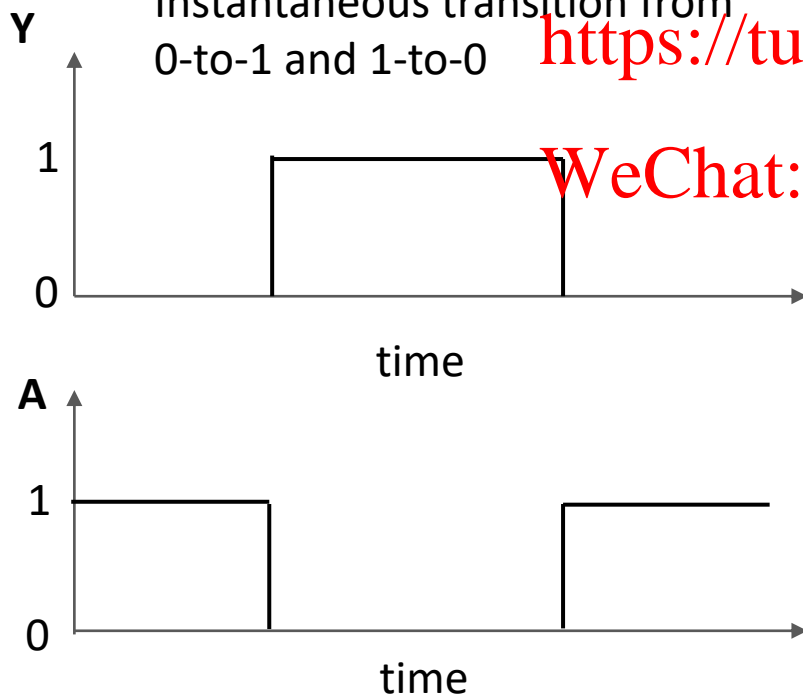Instantaneous transition from
0-to-1 and 1-to-0



Real Property

 Delayed transition from 0-to-1
and 1-to-0




Assignment Project Exam Help

<https://tutorcs.com>


WeChat: cstutorcs

Gate Delay

 Output (Y) transitions from logic 0-to-1 (or 1-to-0)



Real Property

 

Assignment Project Exam Help

<https://tutorcs.com>
WeChat: cstutorcs



t_{lh} = 0-to-1 (low to high) time delay

t_{hl} = 1-to-0 (high to low) time delay

The amount of time (in seconds) needed for the output value to change (**propagation delay, t_d**)

In this course, we'll assume:


$$t_d = t_{lh} = t_{hl}$$

  

FA Component Analysis


Assume, propagation delay (t_d) for each logic gate is 1 nanosecond (ns).

 - When the gate output changes 0-to-1 (or 1-to-0) one ns is required for the output to become stable.



Sum bit analysis


Assume C_i , A, B, S are all initially 0

 

New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0

Sum bit analysis (continued)

 
Assume C_i , A , B , S are all initially 0



New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2

Sum bit analysis (continued)

 
Assume C_i , A , B , S are all initially 0



New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2
0	1	0	1	2

Sum bit analysis (continued)

 Assume C_i , A , B , S are all initially 0




New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2
0	1	0	1	2
0	1	1	0	0

MOS pull-up and pull-down transistor networks are not changing, so the output does not change (even though the inputs have changed)

Sum bit analysis (continued)


Assume C_i , A, B, S are all initially 0

 

New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2
0	1	0	1	2
0	1	1	0	0
1	0	0	1	1

Sum bit analysis (continued)

 Assume C_i , A , B , S are all initially 0




New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2
0	1	0	1	2
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1

MOS pull-up and pull-down transistor networks are not changing, so the output is not changing (even though the inputs have changed)

Sum bit analysis (continued)

 
Assume C_i , A , B , S are all initially 0



New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2
0	1	0	1	2
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1

Sum bit analysis (continued)

Assume C_i , A, B, S are all initially 0

 


New Input Value			S	
C_i	A	B	value	t_d (ns)
0	0	0	0	0
0	0	1	1	2
0	1	0	1	2
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum bit: Worst case analysis

Sum bit is guaranteed to be stable in 2 ns.

In general, follow the longest path from output (S) to inputs and add the gate delays

 
- Easier than analyzing every possible input combination!



Carry-out bit: Worst Case Analysis

Carry-out bit is guaranteed to be stable in 3 ns.

Assignment Project Exam Help
1 ns

 

FA Component: Worst Case Analysis

$\max(\text{Sum } t_d, \text{Carry-out } t_d)$

- All component outputs will be stable in 3 ns

<https://tutorcs.com>

WeChat: cstutorcs

